

Lab Report #3: Simple Processor

Linh Ngo

Brian Dawson

ELC 363 - Computer Engineering Laboratory I

The College of New Jersey

Department of Electrical and Computer Engineering (ECE)



Introduction including Problem Description:

In this lab the students were required to use the Xilinx design package for FPGAs to construct and implement a simple processor. The students needed to study the architecture of the processor in order to process a set a given instruction word formats with 16-bit word-length. The students used an architecture diagram and a controller flow diagram in order to create the processor. The students also used the Von Neuman approach to design the processor as well as implementing machine language code to test the processor.

Results:

a. RTL for each instruction and addressing mode combination

NOT

1. $S0 : IR \leq M(PC)$
2. $S1 : PC \leq PC + 1$
3. $S2 : AC \leq \sim AC$

INCA

1. $S0 : IR \leq M(PC)$
2. $S1 : PC \leq PC + 1$
3. $S3 : AC \leq AC + 1$

JPA (If $AC \leq 0$)

1. $S0 : IR \leq M(PC)$
2. $S1 : PC \leq PC + 1$

JPA (If $AC > 0$ AND $AM = 0$) (DIRECT)

1. $S0 : IR \leq M(PC)$
2. $S1 : PC \leq PC + 1$
3. $S7 : PC \leq IR$ (Address Portion)

JPA (If $AC > 0$ AND $AM = 1$) (INDIRECT)

1. S0 : $IR \leq M(PC)$
2. S1 : $PC \leq PC + 1$
3. S4 : $MA \leq IR$ (Address Portion)
4. S5 : $MD \leq M[MA]$ (Data in memory address)
5. S6 : $PC \leq MD$

STA (AM = 0) (DIRECT)

1. S0 : $IR \leq M(PC)$
2. S1 : $PC \leq PC + 1$
3. S8 : $MA \leq IR$ (Address Portion)
4. S11 : $M[MA] \leq AC$ and $AC \leq 0$

STA (AM = 1) (INDIRECT)

1. S0 : $IR \leq M(PC)$
2. S1 : $PC \leq PC + 1$
3. S8 : $MA \leq IR$ (Address Portion)
4. S9 : $MD \leq M[MA]$ (Data in memory address)
5. S10 : $MA \leq MD$
6. S11 : $M[MA] \leq AC$ and $AC \leq 0$

LDA (AM = 0) (Direct)

1. S0 : $IR \leq M(PC)$
2. S1 : $PC \leq PC + 1$
3. S8 : $MA \leq IR$ (Address Portion)
4. S12 : $MD \leq M[MA]$
5. S16 : $AC \leq MD$

LDA (AM = 1) (Indirect)

1. S0 : $IR \leq M(PC)$
2. S1 : $PC \leq PC + 1$
3. S8 : $MA \leq IR$ (Address Portion)
4. S12 : $MD \leq M[MA]$
5. S13 : $MA \leq M[MD]$
6. S14 : $MD \leq M[MA]$
7. S16 : $AC \leq MD$

ADC (AM = 0) (Direct)

1. S0 : $IR \leq M(PC)$
2. S1 : $PC \leq PC + 1$

3. $S8 : MA \leq IR$ (Address Portion)
4. $S12 : MD \leq M[MA]$
5. $S15 : AC \leq AC + C + MD$

ADC(AM = 1) (Indirect)

1. $S0 : IR \leq M(PC)$
2. $S1 : PC \leq PC + 1$
3. $S8 : MA \leq IR$ (Address Portion)
4. $S12 : MD \leq M[MA]$
5. $S13 : MA \leq M[MD]$
6. $S14 : MD \leq M[MA]$
7. $S15 : AC \leq AC + C + MD$

b. Number of clock cycles for each instruction and addressing mode combination

Instruction with addressing mode	Clock cycles
NOT	3
ADC Indirect	7
ADC Direct	5
JPA Direct	3
JPA Indirect	5
JPA if ACC ≤ 0	2
INCA	3
STA Direct	4
STA Indirect	6
LDA Direct	5
LDA Indirect	7

c. Verilog design code

```
`timescale 1ns / 1ps
module alu(
    input wire [15:0]a,b,
    input wire [2:0]control,
    input wire ci,
    output reg [15:0]y,
    output reg co
);

always @(*) begin
    case(control)
        3'b000: y=~a; //NOTa = Not the Accumulator(Invert it)
        3'b001: {co,y} <= a+b+ci;//Add to input with carry
        3'b010: y = (a + 1); //Increment the Accumulator
        3'b011: y = 0; //Zeroing the Accumulator (Clearing accumulator)
        3'b100: y = b; //Passing B (Used in loading accumulator)
    endcase
end
endmodule

/*****
**/
module controller(
    input [3:0]opcode,
    input pos, //most significant bit
    input clk, reset,
    //input am,

    output reg IR_enable, MD_enable, MA_enable, PC_enable, AC_enable, C_enable,
    output reg MUX1, MUX3,
    output reg [2:0] ALU_control,
    output reg [1:0] MUX2,
    output reg RWn
);

reg [4:0] present_state, next_state;

parameter S00 = 5'h00, S01 = 5'h01, S02 = 5'h02, S03 = 5'h03,S04 = 5'h04,
S05 = 5'h05, S06 = 5'h06, S07 = 5'h07, S08 = 5'h08,S09 = 5'h09, S10 = 5'h0A,
S11 = 5'h0B, S12 = 5'h0C, S13 = 5'h0D,S14 = 5'h0E, S15 = 5'h0F, S16 = 5'h10;

initial begin
    present_state=S00;
end

always@(negedge clk or posedge reset) begin
    if (reset == 1'b1) begin
        present_state=S00;
    end
    else begin
        present_state = next_state;
    end
end
end
```

```

always @(present_state) begin
    case(present_state)

        S00: begin
            IR_enable = 1;
            MD_enable = 0;
            MA_enable = 0;
            PC_enable = 0;
            AC_enable = 0;
            C_enable= 0;
            MUX1 = 0;
            MUX2 = 0;
            MUX3 = 0;
            RWn=1;
            next_state = S01;
        end

        S01: begin
            IR_enable = 0;
            MD_enable = 0;
            MA_enable = 0;
            PC_enable = 1;
            AC_enable = 0;
            C_enable= 0;
            MUX1 = 0;
            MUX2 = 0;
            MUX3 = 0;
            RWn=1;

            if(opcode[3:1] == 3'b000) begin
                next_state = S02;
            end

            else if (opcode[3:1] == 3'b011) begin
                next_state = S03;
            end

            else if (opcode[3:1] == 3'b010) begin
                if (pos == 0) begin
                    if (opcode [0] == 1) begin //look at lsb of opcode
                        next_state = S04;
                    end
                else
                    next_state = S07;
            end
            else
                next_state = S00;
        end

        else
            next_state = S08;
        end

        S02: begin

```

```

        IR_enable = 0;
        MD_enable = 0;
        MA_enable = 0;
        PC_enable = 0;
        AC_enable = 1;
        C_enable= 0;
        MUX1 = 0;
        MUX2 = 0;
        MUX3 = 0;
        RWn=1;
        next_state = S00;
        ALU_control[2:0]= 0;
    end

```

```

S03: begin
    IR_enable = 0;
    MD_enable = 0;
    MA_enable = 0;
    PC_enable = 0;
    AC_enable = 1;
    C_enable= 0;
    MUX1 = 0;
    MUX2 = 0;
    MUX3 = 0;
    RWn=1;
    next_state = S00;
    ALU_control[2:0]= 2;
end

```

```

end

```

```

S04: begin
    IR_enable = 0;
    MD_enable = 0;
    MA_enable = 1;
    PC_enable = 0;
    AC_enable = 0;
    C_enable= 0;
    MUX1 = 0;
    MUX2 = 0;
    MUX3 = 0;
    RWn=1;
    next_state = S05;
end

```

```

S05: begin
    IR_enable = 0;
    MD_enable = 1;
    MA_enable = 0;
    PC_enable = 0;
    AC_enable = 0;
    C_enable= 0;
    MUX1 = 0;
    MUX2 = 0;
    MUX3 = 1;
    RWn=1;
    next_state = S06;
end

```

```

S06: begin
    IR_enable = 0;
    MD_enable = 0;
    MA_enable = 0;
    PC_enable = 1;
    AC_enable = 0;
    C_enable= 0;
    MUX1 = 0;
    MUX2 = 2;
    MUX3 = 0;
    RWn=1;
    next_state = S00;
end

S07: begin
    IR_enable = 0;
    MD_enable = 0;
    MA_enable = 0;
    PC_enable = 1;
    AC_enable = 0;
    C_enable= 0;
    MUX1 = 0;
    MUX2 = 1;
    MUX3 = 0;
    RWn=1;
    next_state = S00;
end

S08: begin
    IR_enable = 0;
    MD_enable = 0;
    MA_enable = 1;
    PC_enable = 0;
    AC_enable = 0;
    C_enable= 0;
    MUX1 = 0;
    MUX2 = 0;
    MUX3 = 0;
    RWn=1;

    if (opcode[3:1] == 3'b100) begin
        if (opcode[0] ==1) begin
            next_state = S09;
        end
        else if (opcode[0] ==0) begin
            next_state = S11;
        end
    end
    else
        next_state = S12;
    end

S09: begin
    IR_enable = 0;
    MD_enable = 1;
    MA_enable = 0;

```



```

        PC_enable = 0;
        AC_enable = 0;
        C_enable= 0;
        MUX1 = 0;
        MUX2 = 0;
        MUX3 = 1;
        RWn=1;
        next_state = S10;
    end

S10: begin
    IR_enable = 0;
    MD_enable = 0;
    MA_enable = 1;
    PC_enable = 0;
    AC_enable = 0;
    C_enable= 0;
    MUX1 = 1;
    MUX2 = 0;
    MUX3 = 0;
    RWn=1;
    next_state = S11;
end

S11: begin
    IR_enable = 0;
    MD_enable = 0;
    MA_enable = 0;
    PC_enable = 0;
    AC_enable = 1;
    C_enable= 0;
    MUX1 = 0;
    MUX2 = 0;
    MUX3 = 1;
    ALU_control[2:0]=3;
    #3 RWn=0;
    next_state = S00;
end

S12: begin
    IR_enable = 0;
    MD_enable = 1;
    MA_enable = 0;
    PC_enable = 0;
    AC_enable = 0;
    C_enable= 0;
    MUX1 = 0;
    MUX2 = 0;
    MUX3 = 1;
    RWn=1;

    if (opcode[0] == 1) begin
        next_state = S13;
    end
    else begin
        if (opcode[3:1] ==3'b001)
            next_state = S15;
        end
    end
end

```

```

        else
            next_state = S16;
        end
    end
end

S13: begin
    IR_enable = 0;
    MD_enable = 0;
    MA_enable = 1;
    PC_enable = 0;
    AC_enable = 0;
    C_enable = 0;
    MUX1 = 1;
    MUX2 = 0;
    MUX3 = 0;
    RWn=1;
    next_state = S14;
end

S14: begin
    IR_enable = 0;
    MD_enable = 1;
    MA_enable = 0;
    PC_enable = 0;
    AC_enable = 0;
    C_enable = 0;
    MUX1 = 0;
    MUX2 = 0;
    MUX3 = 1;
    RWn=1;

    if (opcode[3:1] == 3'b001) begin
        next_state = S15;
    end
    else
        next_state = S16;
    end
end

S15: begin
    IR_enable = 0;
    MD_enable = 0;
    MA_enable = 0;
    PC_enable = 0;
    AC_enable = 1;
    C_enable = 1;
    MUX1 = 0;
    MUX2 = 0;
    MUX3 = 0;
    RWn=1;
    ALU_control[2:0]=1;
    next_state = S00;
end

S16: begin
    IR_enable = 0;

```

```

        MD_enable = 0;
        MA_enable = 0;
        PC_enable = 0;
        AC_enable = 1;
        C_enable = 0;
        MUX1 = 0;
        MUX2 = 0;
        MUX3 = 0;
        RWn=1;
        ALU_control[2:0]=4;
        next_state = S00;
    end

endcase
end

endmodule

/*****
*/
module data_path(
    input CLK,
    input reset,

    input MD_enable,
    input IR_enable,
    input AC_enable,
    input PC_enable,
    input MA_enable,
    input C_enable,

    input [2:0]alu_control,
    input mux1,
    input mux3,
    input [1:0]mux2,

    input [15:0] RD,

    output reg [15:0] WD,
    output reg [11:0] A,
    output reg [15:0] IR

);

    reg [15:0] AC;
    reg [15:0] MD;
    reg [11:0] PC;
    reg [11:0] MA;
    reg C;

    wire [15:0] y;
    wire co;

    initial begin
        if( reset == 1'b1) begin
            PC[11:0] = 12'h000;

```

```

        MA[11:0] = 12'h000;
        MD[15:0] = 16'h0000;
        AC[15:0] = 16'h0000;
        IR[15:0] = 16'h0000;
        C = 1'b0;
        A[11:0] = 12'h000;
    end
end

always @ (posedge CLK ) begin
    if ( MD_enable == 1'b1 ) begin
        #1 MD = RD;
    end
    else if ( IR_enable == 1'b1 ) begin
        #1 IR = RD;
    end
end

//Call ALU... And reassigning AC when needed
alu op3 ( AC, MD, alu_control, C, y, co);
always @ (posedge CLK ) begin
    if ( AC_enable == 1'b1) begin
        #1 AC = y;
    end
    if (C_enable == 1'b1 ) begin
        C = co;
    end
end

//Mux 1
always @ (posedge CLK) begin
    if ( mux1 == 1'b0 && MA_enable == 1) begin
        MA = IR[11:0];
    end
    else if ( mux1 == 1'b1 && MA_enable == 1 ) begin
        MA = MD[11:0];
    end
end

//Mux 2
always @ (posedge CLK) begin
    if ( mux2 == 2'b00 && PC_enable == 1) begin
        PC = PC + 1;
    end
    else if ( mux2 == 2'b01 && PC_enable == 1 ) begin
        PC = IR[11:0];
    end
    else if ( mux2 == 2'b10 && PC_enable == 1 ) begin
        PC = MD[11:0];
    end
end

//Mux 3
always @ (posedge CLK) begin
    if ( mux3 == 1'b0 ) begin
        A = PC;
    end
end

```

```

        end
        else if ( mux3 == 1'b1 ) begin
            A = MA;
        end
    end

    end

    always @ (posedge CLK) begin
        WD = AC;
    end

endmodule

/*****
**/
module simpleCPU(
    input CLK, reset,
    input [15:0] RD,
    output [15:0] WD,
    output RWn,
    output [11:0] A
);

    wire mux1,mux3,IR_enable,MD_enable,AC_enable,MA_enable,PC_enable, C_enable;
    wire [1:0] mux2;
    wire[2:0]alu_control;
    wire [15:0] IR;

    data_path m2( CLK, reset, MD_enable, IR_enable, AC_enable, PC_enable, MA_enable,
C_enable,
    alu_control[2:0], mux1, mux3, mux2[1:0], RD[15:0], WD[15:0], A[11:0], IR[15:0]);

    controller m3( IR[15:12], WD[15], CLK, reset, IR_enable, MD_enable, MA_enable, PC_enable,
AC_enable, C_enable,
    mux1, mux3,alu_control[2:0],mux2[1:0], RWn );

endmodule

```

d. Verilog test bench code

```
`timescale 1ns / 1ps
module procssor_tb;
// Inputs
    reg CLK=0;
    reg reset=1;
    reg [15:0] RD;
    wire [11:0]A;
    wire [15:0] WD;
    wire RWn;
    reg [15:0] memory[0:18];

    initial begin
        $readmemh("C:/Users/ngoll.LIONS.006/Desktop/memory.dat", memory);
    end

    // Instantiate the Unit Under Test (UUT)
    simpleCPU uut (
        .CLK(CLK),
        .reset(reset),
        .RD(RD),
        .WD(WD),
        .A(A),
        .RWn(RWn)
    );

    initial begin
        reset <= 1;
        #1 reset <=0;
    end

    always begin
        #2 CLK = ~CLK;
    end

    always @* begin
        if (RWn == 1'b0) begin
            memory[A] = WD;
        end
        else begin
            if (RWn == 1'b1)
                RD = memory[A];
        end
    end

    initial #250 $finish;

endmodule
```




e. Assembly language test program

```
not
sta &0
inca
adc &0
adc * &17
sta * &16
lda &1
jpa $0
lda * &18
jpa $13
not
not
jpa * $14
not
(14) 4371
(15) 4372
not
(17) 18
(18) 4113
```


f. Machine language test program

@000	0000
@001	8000
@002	6000
@003	2000
@004	3011
@005	9010
@006	A001
@007	4000
@008	B012
@009	400C
@00A	0000
@00B	0000
@00C	500D
@00D	0000
@00E	1113
@00F	1114
@010	0000
@011	0012
@012	1011



g. Waveforms from verification of design

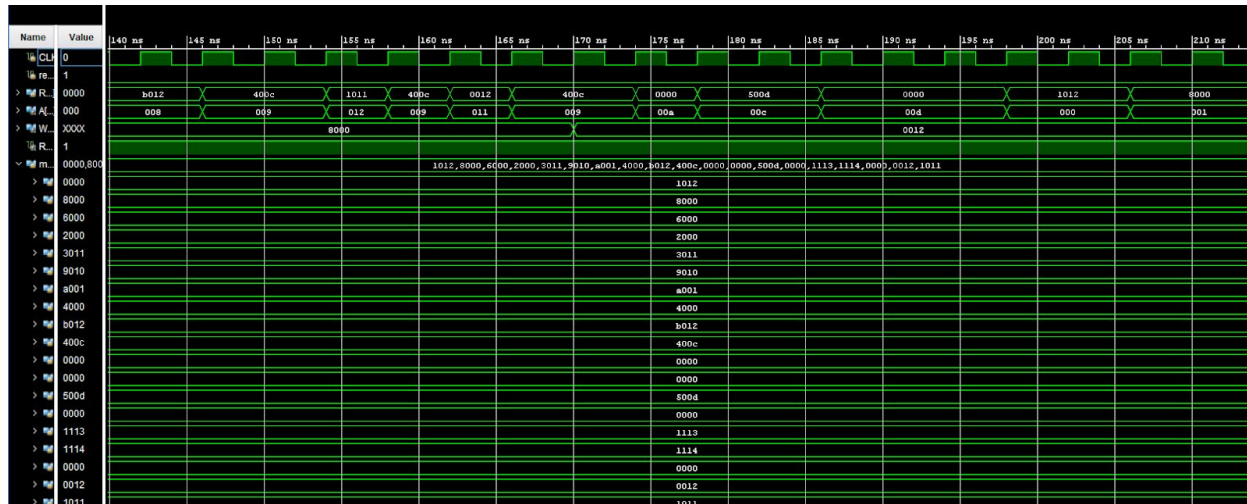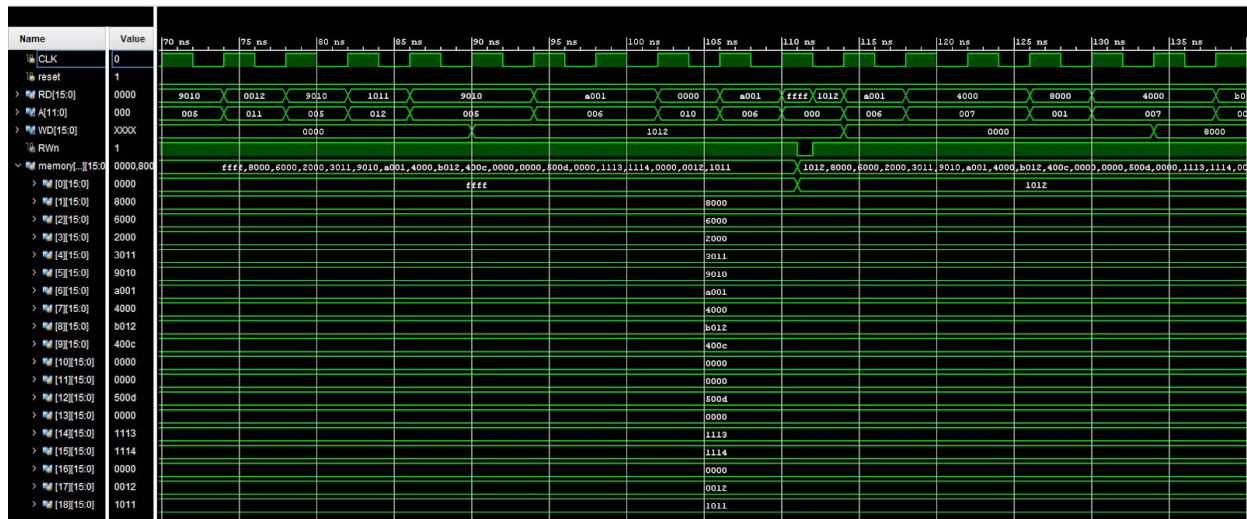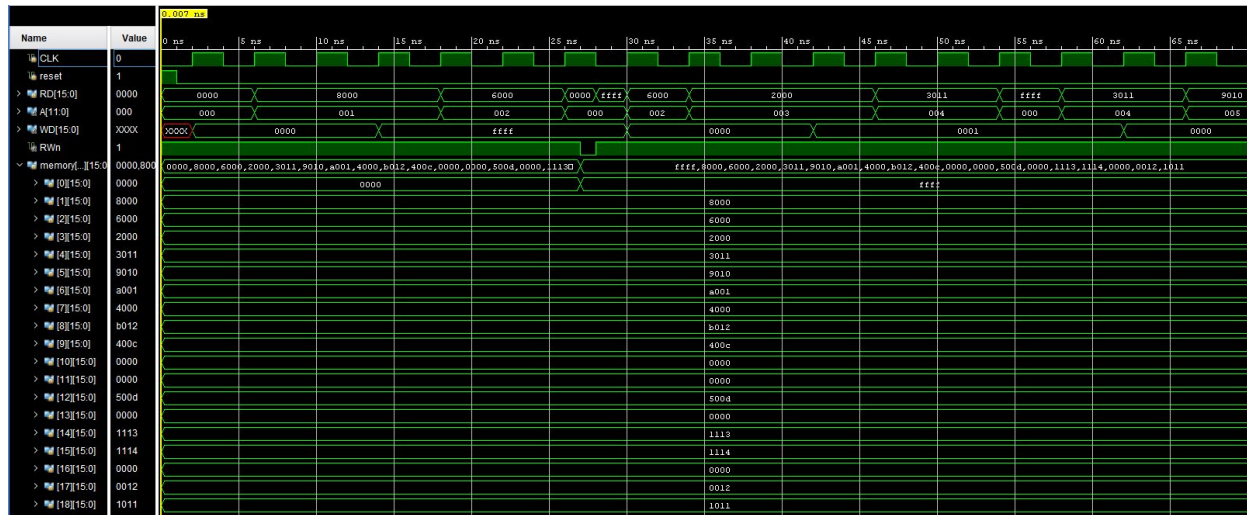

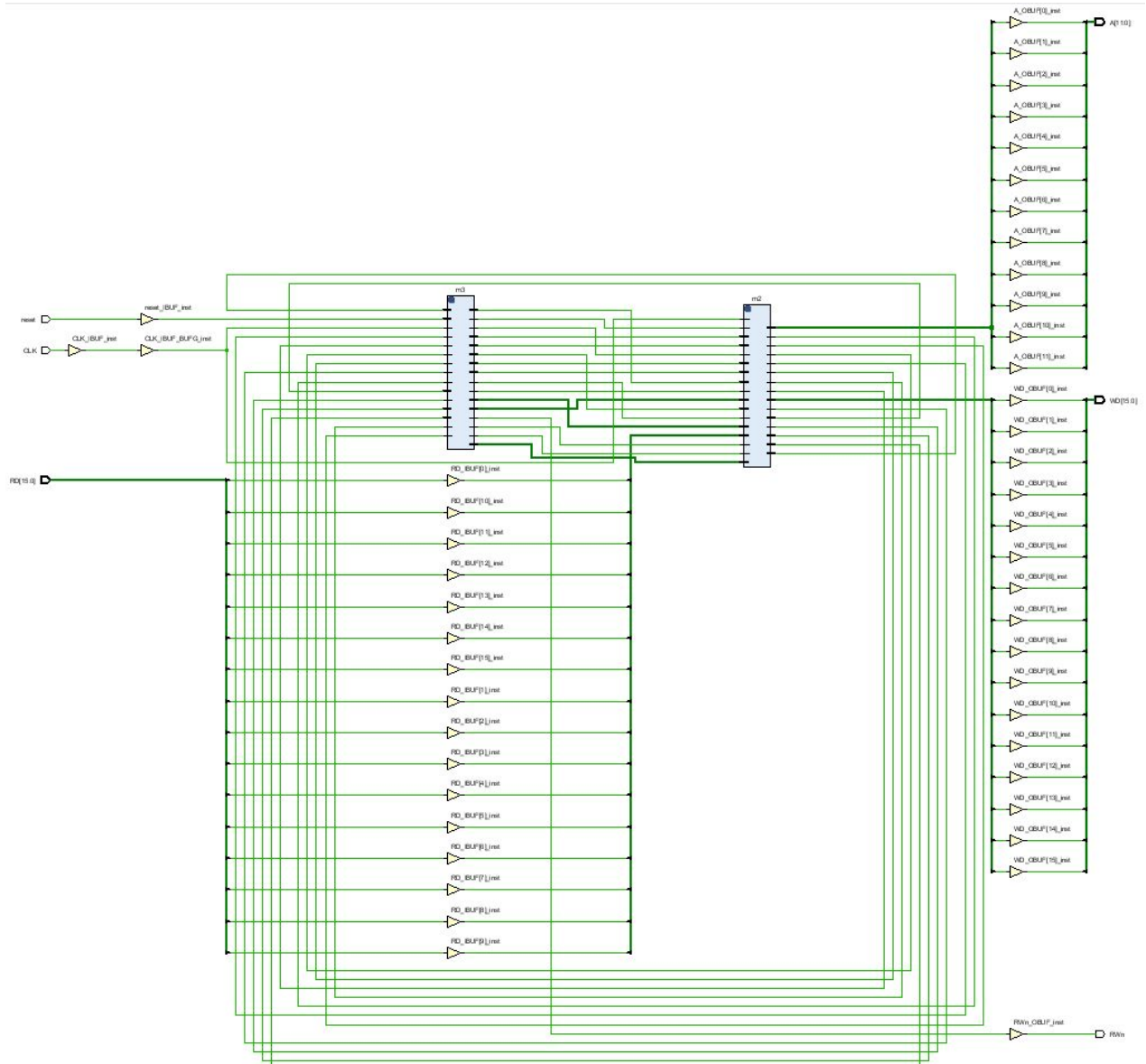- h. Design schematic from Xilinx synthesis of design with no area constraint and clock period of 1 μ S as the timing constraint



i. Routed Design

  

j. Post place and route timing report

Copyright 1986-2017 Xilinx, Inc. All Rights Reserved.

```
-----
| Tool Version : Vivado v.2017.4 (win64) Build 2086221 Fri Dec 15 20:55:39 MST 2017
| Date        : Sun Nov  3 13:12:13 2019
| Host        : STEM241-07 running 64-bit major release (build 9200)
| Command     : report_timing_summary -max_paths 10 -file simpleCPU_timing_summary_routed.rpt
-rpx simpleCPU_timing_summary_routed.rpx -warn_on_violation
| Design      : simpleCPU
| Device      : 7k70t-fbv676
| Speed File  : -1 PRODUCTION 1.12 2017-02-17
-----
```

Timing Summary Report

Timer Settings

```
-----
--
| Timer Settings
| -----
--
Enable Multi Corner Analysis      : Yes
Enable Pessimism Removal          : Yes
Pessimism Removal Resolution      : Nearest Common Node
Enable Input Delay Default Clock  : No
Enable Preset / Clear Arcs       : No
Disable Flight Delays             : No
Ignore I/O Paths                 : No
Timing Early Launch at Borrowing Latches : false
```

Corner Name	Analyze Max Paths	Analyze Min Paths
Slow	Yes	Yes
Fast	Yes	Yes

check_timing report

Table of Contents

- ```

1. checking no_clock
2. checking constant_clock
3. checking pulse_width_clock
4. checking unconstrained_internal_endpoints
5. checking no_input_delay
6. checking no_output_delay
7. checking multiple_clock
8. checking generated_clocks
9. checking loops
10. checking partial_input_delay
11. checking partial_output_delay
12. checking latch_loops
```

#### 1. checking no\_clock

```

There are 107 register/latch pins with no clock driven by root clock pin: CLK (HIGH)
```

There are 17 register/latch pins with no clock driven by root clock pin:  
m3/ALU\_control\_reg[0]/Q (HIGH)

There are 17 register/latch pins with no clock driven by root clock pin:  
m3/ALU\_control\_reg[1]/Q (HIGH)

There are 17 register/latch pins with no clock driven by root clock pin:  
m3/ALU\_control\_reg[2]/Q (HIGH)

There are 19 register/latch pins with no clock driven by root clock pin:  
m3/FSM\_sequential\_present\_state\_reg[0]/Q (HIGH)

There are 19 register/latch pins with no clock driven by root clock pin:  
m3/FSM\_sequential\_present\_state\_reg[1]/Q (HIGH)

There are 19 register/latch pins with no clock driven by root clock pin:  
m3/FSM\_sequential\_present\_state\_reg[2]/Q (HIGH)

There are 19 register/latch pins with no clock driven by root clock pin:  
m3/FSM\_sequential\_present\_state\_reg[3]/Q (HIGH)

There are 19 register/latch pins with no clock driven by root clock pin:  
m3/FSM\_sequential\_present\_state\_reg[4]/Q (HIGH)

## 2. checking constant\_clock

-----

There are 0 register/latch pins with constant\_clock.

## 3. checking pulse\_width\_clock

-----

There are 0 register/latch pins which need pulse\_width check

## 4. checking unconstrained\_internal\_endpoints

-----

There are 220 pins that are not constrained for maximum delay. (HIGH)

There are 0 pins that are not constrained for maximum delay due to constant clock.

## 5. checking no\_input\_delay

-----

There are 17 input ports with no input delay specified. (HIGH)

There are 0 input ports with no input delay but user has a false path constraint.

## 6. checking no\_output\_delay

-----

There are 29 ports with no output delay specified. (HIGH)

There are 0 ports with no output delay but user has a false path constraint

There are 0 ports with no output delay but with a timing clock defined on it or propagating through it

## 7. checking multiple\_clock

-----

There are 0 register/latch pins with multiple clocks.

## 8. checking generated\_clocks

-----

There are 0 generated clocks that are not connected to a clock source.

9. checking loops

There are 0 combinational loops in the design.

10. checking partial\_input\_delay

There are 0 input ports with partial input delay specified.

11. checking partial\_output\_delay

There are 0 ports with partial output delay specified.

12. checking latch\_loops

There are 0 combinational latch loops in the design through latch input

Design Timing Summary

| WNS(ns)               |                     | TNS(ns)               |                     | TNS Failing Endpoints |          | TNS Total Endpoints    |                      | WHS(ns)                |                      | THS(ns)                |                      |
|-----------------------|---------------------|-----------------------|---------------------|-----------------------|----------|------------------------|----------------------|------------------------|----------------------|------------------------|----------------------|
| THS Failing Endpoints | THS Total Endpoints | THS Failing Endpoints | THS Total Endpoints | WPWS(ns)              | TPWS(ns) | TPWS Failing Endpoints | TPWS Total Endpoints | TPWS Failing Endpoints | TPWS Total Endpoints | TPWS Failing Endpoints | TPWS Total Endpoints |
| NA                    | NA                  | NA                    | NA                  | NA                    | NA       | NA                     | NA                   | NA                     | NA                   | NA                     | NA                   |
| NA                    | NA                  | NA                    | NA                  | NA                    | NA       | NA                     | NA                   | NA                     | NA                   | NA                     | NA                   |

All user specified timing constraints are met.

Clock Summary

| Clock | Waveform(ns)    | Period(ns) | Frequency(MHz) |
|-------|-----------------|------------|----------------|
| CLK   | {0.000 500.000} | 1000.000   | 1.000          |

Intra Clock Table

```

Clock WNS(ns) TNS(ns) TNS Failing Endpoints TNS Total Endpoints
WHS(ns) THS(ns) THS Failing Endpoints THS Total Endpoints WPWS(ns) TPWS(ns)
TPWS Failing Endpoints TPWS Total Endpoints

--
Inter Clock Table

--

From Clock To Clock WNS(ns) TNS(ns) TNS Failing Endpoints TNS Total
Endpoints WHS(ns) THS(ns) THS Failing Endpoints THS Total Endpoints

--
Other Path Groups Table

--

Path Group From Clock To Clock WNS(ns) TNS(ns) TNS Failing Endpoints TNS
Total Endpoints WHS(ns) THS(ns) THS Failing Endpoints THS Total Endpoints

--
Timing Details

--

```

## Discussion:

In this lab we were able to correctly implement all of the components of the lab. The various components of the design code, the ALU, controller, and datapath all worked correctly. They produced the correct waveforms. The testbench also was correct. The fully implemented processor's waveforms were correct. The RTL's were correct as well as the number of clock cycles for each instruction and addressing type. The assembly language program created the

correct machine language program. The design schematic from the synthesis with no area constraint was right as well as the routed design and timing report.

### **Conclusions:**

All of the components of the lab worked as expected. The ALU, control, and datapath all worked correctly individually. They produced the correct outputs and waveforms. They also then worked together once paired with the testbench. This shows that the processor works as intended. All of the diagrams were correct and showed the right information.